



IC-UNICAMP

MC 613

IC/Unicamp


Prof Guido Araújo

Prof Mario Côrtes


Prof Sandro Rigo

Máquinas de Estado

Forma geral de um circuito síncrono

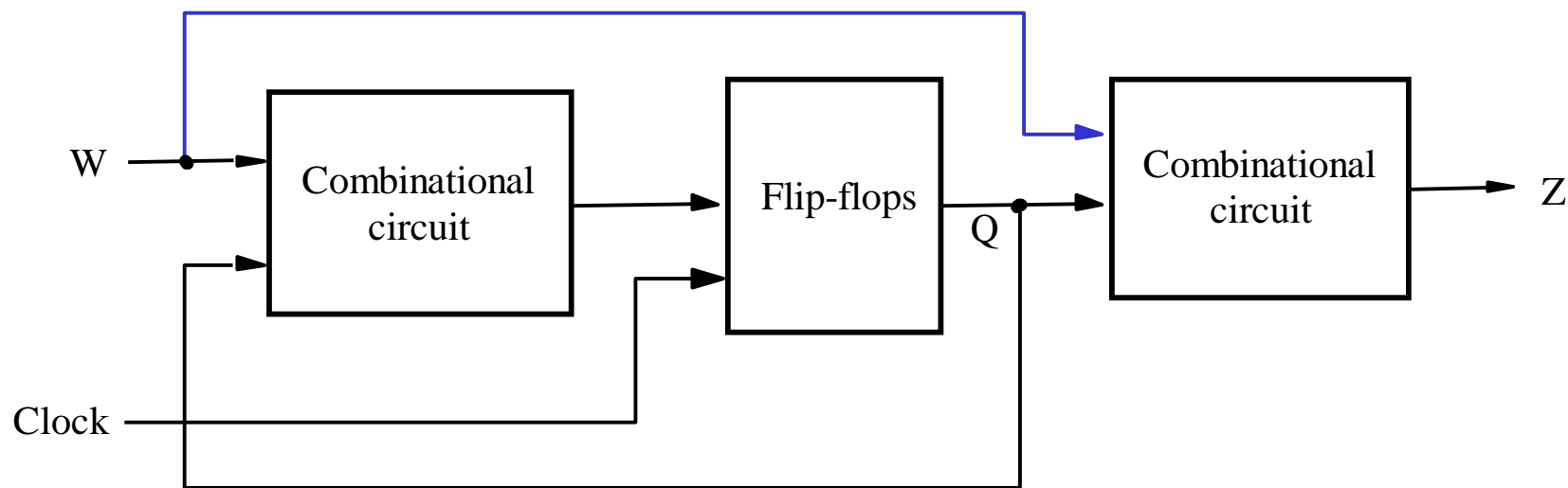


Máquina de Moore

 


Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Diagrama de Estados

 


Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

Implementação

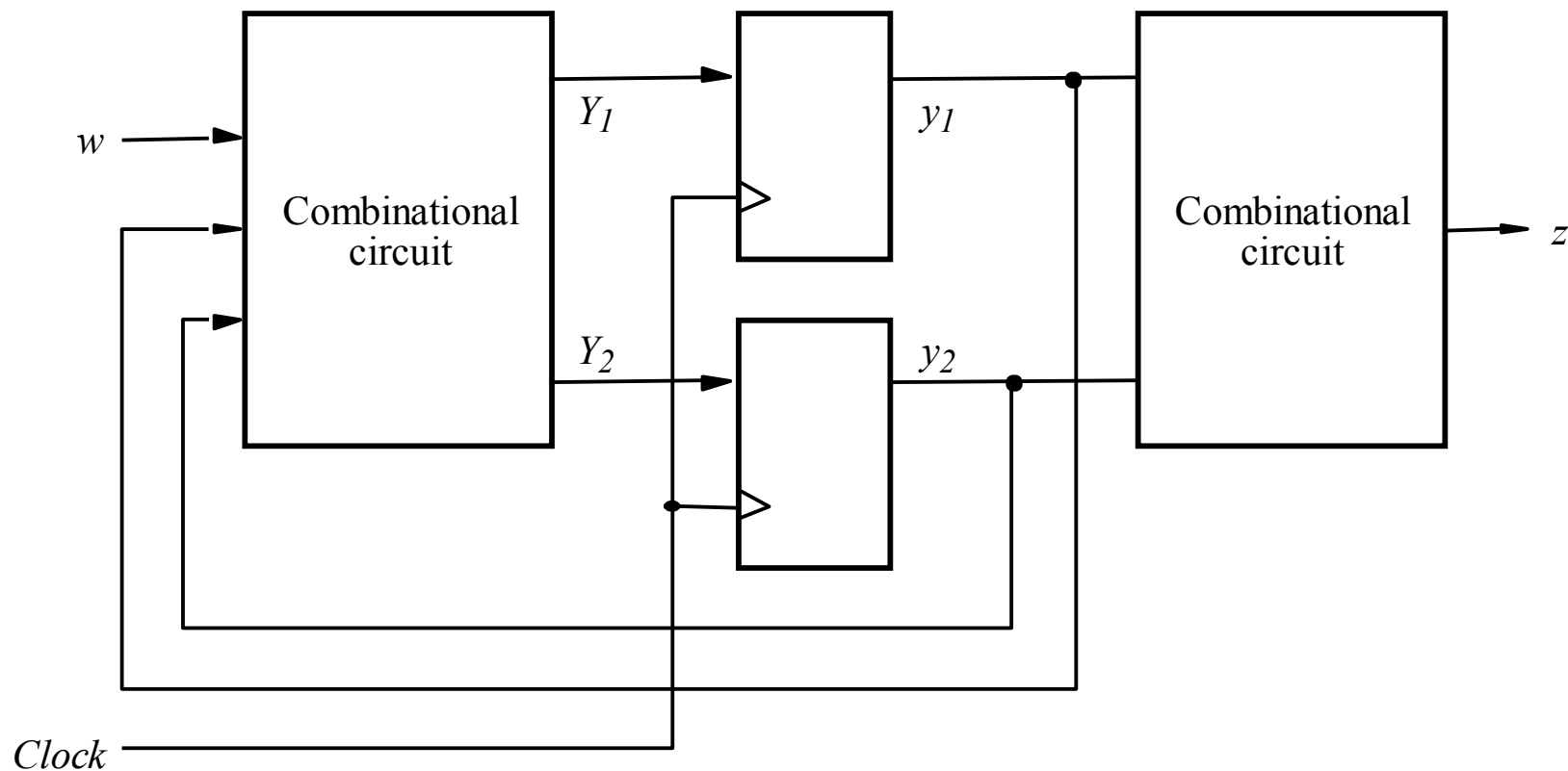

Atribuição de Estado

 

A
B
C

Present state $y_2 y_1$	Next state		Output z
	$w = 0$	$w = 1$	
	$Y_2 Y_1$	$Y_2 Y_1$	
00	00	01	0
01	00	10	0
10	00	10	1
11	dd	dd	d

Derivação das expressões lógicas

		2	1		
	w				
		00	01	11	10
0		0	0	d	0
1		1	0	d	0

Ignoring don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

Using don't cares

$$Y_1 = w\bar{y}_1\bar{y}_2$$

			y ₂	y ₁	
	w				
		00	01	11	10
0		0	0	d	0
1		0	1	d	1

$$Y_2 = wy_1\bar{y}_2 + w\bar{y}_1y_2$$


$$\begin{aligned} Y_2 &= wy_1 + w\bar{y}_1y_2 \\ &= w(y_1 + y_2) \end{aligned}$$

			y ₁	
	y ₂			
		0	1	
0		0	0	
1		1	d	


$$z = \bar{y}_1y_2$$

$$z = y_2$$

Circuito sequencial

 

Timing diagram

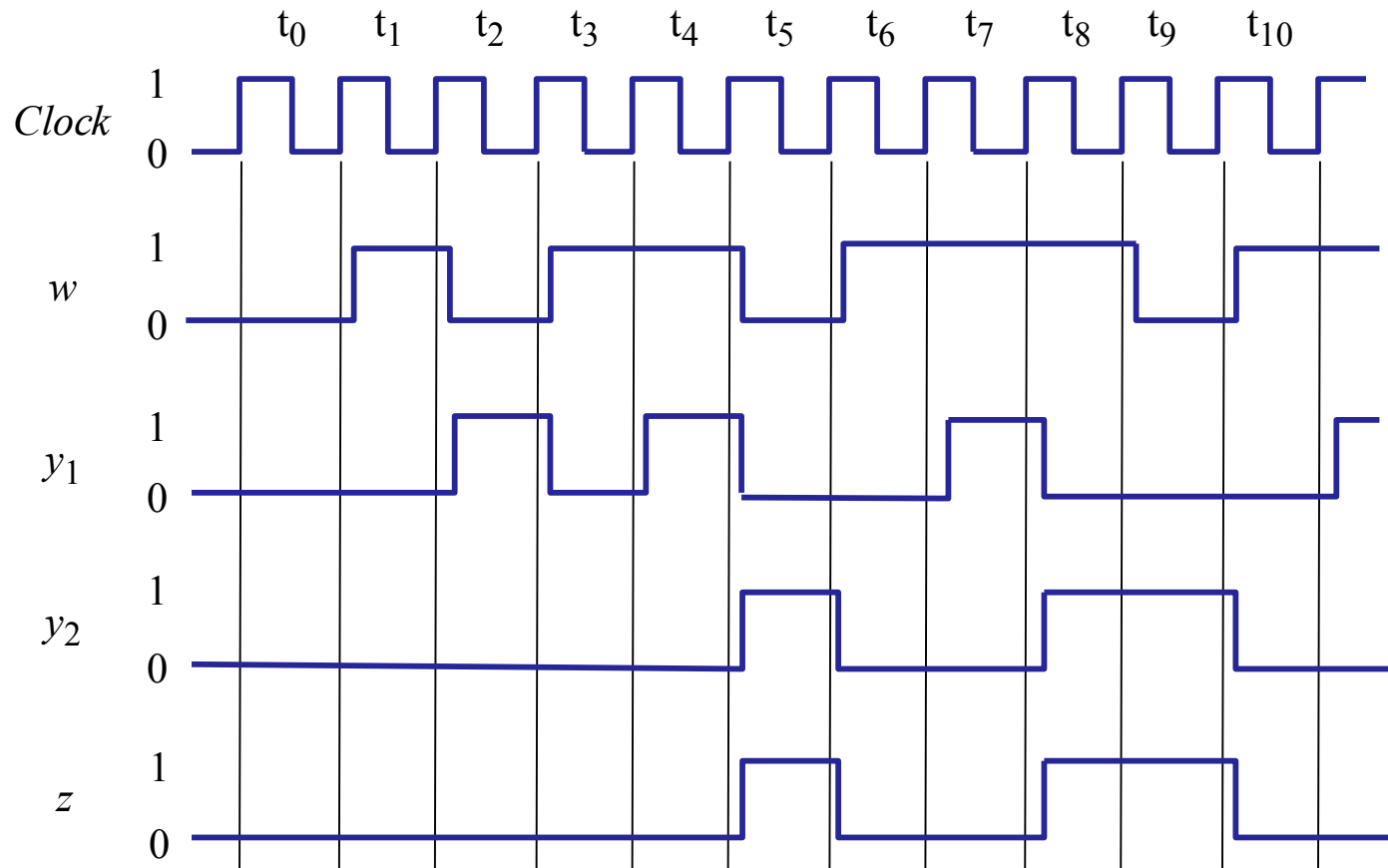



FSM de Moore

```
USE ieee.std_logic_1164.all;

ENTITY simple IS
    PORT (Clock, Resetn, w : IN          STD_LOGIC;
          z                : OUT        STD_LOGIC );
END simple;

ARCHITECTURE Behavior OF simple IS
    TYPE State_type IS (A, B, C); -- Tipo Enumerado para
                                   -- definir os Estados

    SIGNAL y : State_type;
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN -- A é o estado inicial
            y <= A;
        ELSIF (Clock'EVENT AND Clock = '1') THEN


con't ...
```

FSM de Moore





IC-UNICAMP


 
```
CASE y IS
  WHEN A =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= B;
    END IF;
  WHEN B =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= C;
    END IF;
  WHEN C =>
    IF w = '0'
      THEN y <= A;
      ELSE y <= C;
    END IF;
END CASE;
END IF;
END PROCESS;
z <= '1' WHEN y = C ELSE '0';
END Behavior;
```



FSM de Moore - Simulação

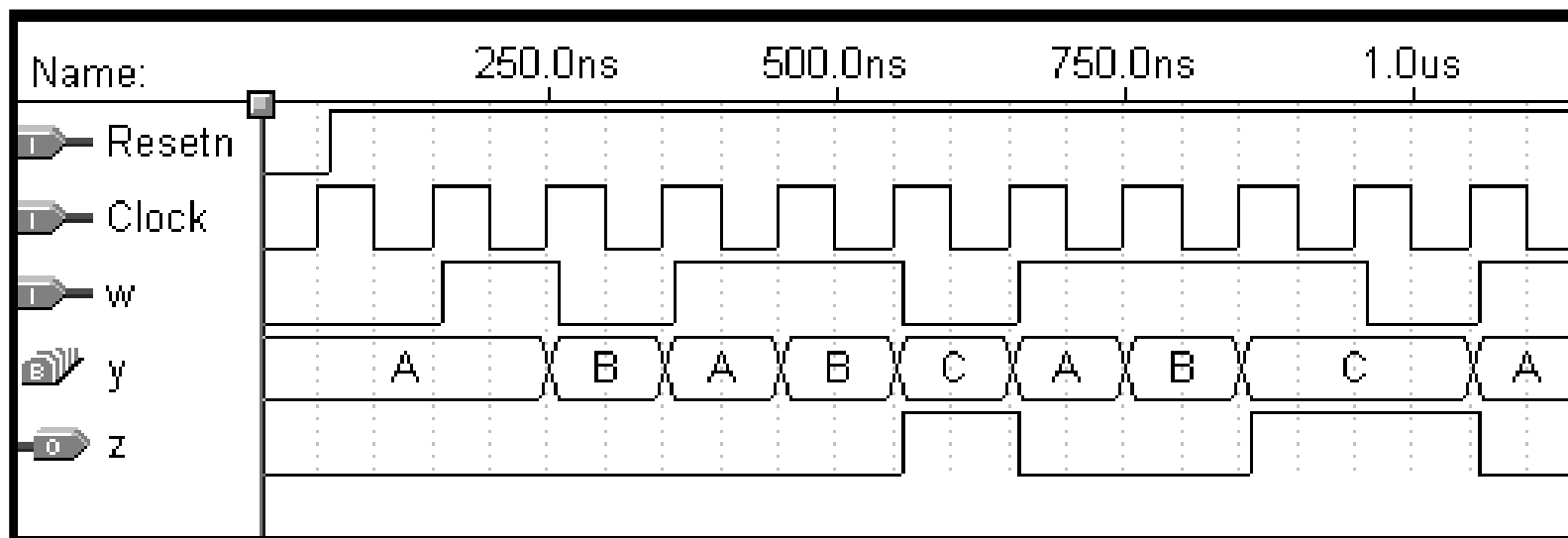 

FSM de Moore - Simulação

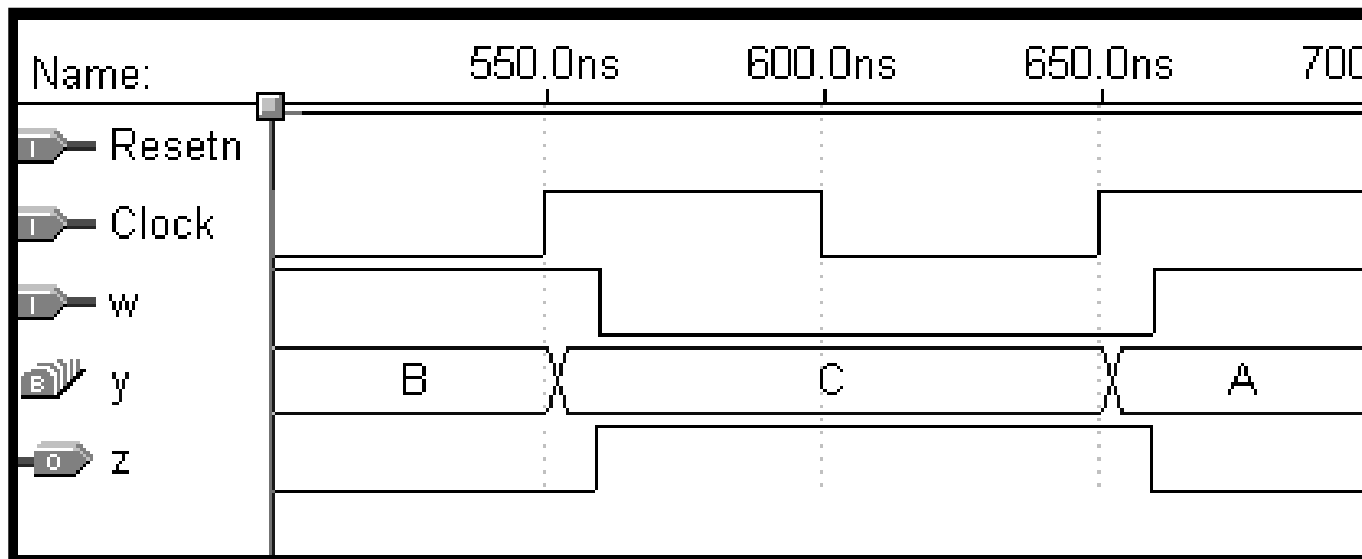 

Codificação Alternativa (2 processos)

```
USE ieee.std_logic_1164.all;
```

```
ENTITY simple IS
```

```
    PORT (Clock, Resetn, w : IN      STD_LOGIC;  
          z                : OUT    STD_LOGIC );
```

```
END simple;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C);
```

```
SIGNAL y_present, y_next : State_type;
```

FSM de Moore



IC-UNICAMP

Codificação Alternativa (2 processos)

BEGIN

PROCESS (w, **y_present**)

BEGIN

CASE y_present IS

WHEN A =>

IF w = '0' THEN

y_next <= A;

ELSE

y_next <= B;

END IF;

WHEN B =>


IF w = '0' THEN

y_next <= A;

ELSE

y_next <= C;

END IF;

 



FSM de Moore - Codificação Alternativa

```

WHEN C =>
    IF w = '0' THEN
        y_next <= A;
    ELSE
        y_next <= C;
    END IF;

```

```

    END CASE;
END PROCESS;

```

```

PROCESS (Clock, Resetn)
BEGIN

```

```

    IF Resetn = '0' THEN

```

```

        y_present <= A;

```

```

    ELSIF (Clock'EVENT AND Clock = '1') THEN

```

```

        y_present <= y_next;

```

```

    END IF;

```

```

END PROCESS;

```

```


    z <= '1' WHEN y_present = C ELSE '0';

```

```

END Behavior;

```

 

FSM - Especificando a Atribuição de Estados

ARCHITECTURE Behavior OF simple IS

```
TYPE State_TYPE IS (A, B, C);
```

```
ATTRIBUTE ENUM_ENCODING : STRING;
```

```
ATTRIBUTE ENUM_ENCODING OF State_type: TYPE IS "00 01  
11";
```

```
SIGNAL y_present, y_next : State_type;
```

```
BEGIN
```

```
con't ...
```

- Obs: Atributo Enum_Encoding é específico da ferramenta Quartus. Esta solução pode não funcionar em outras ferramentas CAD

FSM - Especificando a Atribuição de Estados

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY simple IS
    PORT ( Clock, Resetn, w : IN          STD_LOGIC;
          z                  : OUT   STD_LOGIC );
END simple;
ARCHITECTURE Behavior OF simple IS
    SIGNAL y_present, y_next : STD_LOGIC_VECTOR(1 DOWNTO 0);
    CONSTANT A      : STD_LOGIC_VECTOR(1 DOWNTO 0) := "00";
    CONSTANT B      : STD_LOGIC_VECTOR(1 DOWNTO 0) := "01";
    CONSTANT C      : STD_LOGIC_VECTOR(1 DOWNTO 0) := "11";
BEGIN
    PROCESS ( w, y_present )
    BEGIN
        CASE y_present IS
            WHEN A =>
                IF w = '0' THEN y_next <= A;
                ELSE y_next <= B;
                END IF;
            -- WHEN B =>
            -- WHEN C =>
        END CASE;
    END PROCESS;
END Behavior;
```

... con't

FSM - Especificando a Atribuição de Estados


```

    WHEN B =>
        IF w = '0' THEN y_next <= A;
        ELSE y_next <= C;
        END IF;
    WHEN C =>
        IF w = '0' THEN y_next <= A;
        ELSE y_next <= C;
        END IF;
    WHEN OTHERS =>
        y_next <= A;
    END CASE;
END PROCESS;

PROCESS ( Clock, Resetn )
BEGIN
    IF Resetn = '0' THEN
        y_present <= A;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
        y_present <= y_next;
    END IF;
END PROCESS;


z <= '1' WHEN y_present = C ELSE '0';

```

 

END Behavior;

Máquina de Mealy

 

FSM de Mealy

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY mealy IS  
    PORT (Clock, Resetn, w: IN STD_LOGIC;  
          z: OUT STD_LOGIC );  
END mealy;
```

... con' t



FSM de Mealy

ARCHITECTURE Behavior OF mealy IS

TYPE State_type IS (A, B);

SIGNAL y : State_type;

BEGIN

PROCESS (Resetn, Clock)

BEGIN

IF Resetn = '0' THEN y <= A;

ELSIF (Clock'EVENT AND Clock = '1') THEN

CASE y IS

WHEN A =>

IF w = '0' THEN y <= A;

ELSE y <= B;

END IF;

WHEN B =>

IF w = '0' THEN y <= A;


ELSE y <= B;

END IF;


END CASE;

END IF;

END PROCESS;

 

FSM de Mealy

 

```

PROCESS ( y, w )
BEGIN
    CASE y IS
        WHEN A =>
            z <= '0' ;
        WHEN B =>
            z <= w ;
    END CASE ;
END PROCESS ;
END Behavior ;
  
```